

Parallel Circuit Table

Number of Light Bulbs in Parallel	Circuit Diagram	Relative Brightness of bulbs (use words like brightest, least bright, etc.)
2		
3		