

Series Circuit Table

Number of Light Bulbs	Circuit Diagram	Relative Brightness of bulbs (use words like brightest, least bright, etc.)
1		
2		
3		